

**Bilkent University**

**Electrical and Electronics Department**

**EE313-02 Lab 4 Preliminary Report:**

**“Wide-Band Amplifier with Feedback”**

01/12/2024

Fatih Mehmet Çetin - 22201689

## **Introduction:**

This lab's main aim is designing a two-stage amplifier with feedback to achieve a low output impedance and a flat gain.

## **Simulation & Analysis:**

Here are some specifications which were given to us in the lab manual (**Figure 1**):

Specifications:

Source impedance:  $500\Omega$

Load impedance:  $47\Omega$

Mid band voltage Gain:  $20\text{ dB} \pm 0.5\text{ dB}$

Bandwidth ( $-3\text{ dB}$ ): at least  $2\text{ KHz}$  to  $2\text{ MHz}$  (by CNTL-Click in AC analysis)

Supply voltage:  $12\text{ V}$  (single supply)


Maximum current consumption:  $70\text{ mA}$  from the supply voltage

Undistorted peak-to-peak output voltage:  $2V_{pp}$  at  $200\text{ KHz}$ .

Distortion at the output: Harmonics less than  $-30\text{ dBc}$  at  $200\text{ KHz}$   $2V_{pp}$  output voltage (the difference between the fundamental and the highest harmonic in FFT window)

**Figure 1: The Specifications of the Circuit**

Here you can see my final circuit for this lab (**Figure 2**). As you can see the source impedance is  $500\Omega$ , the load impedance is  $47\Omega$ . The DC supply voltage is  $12\text{ Volts}$ .

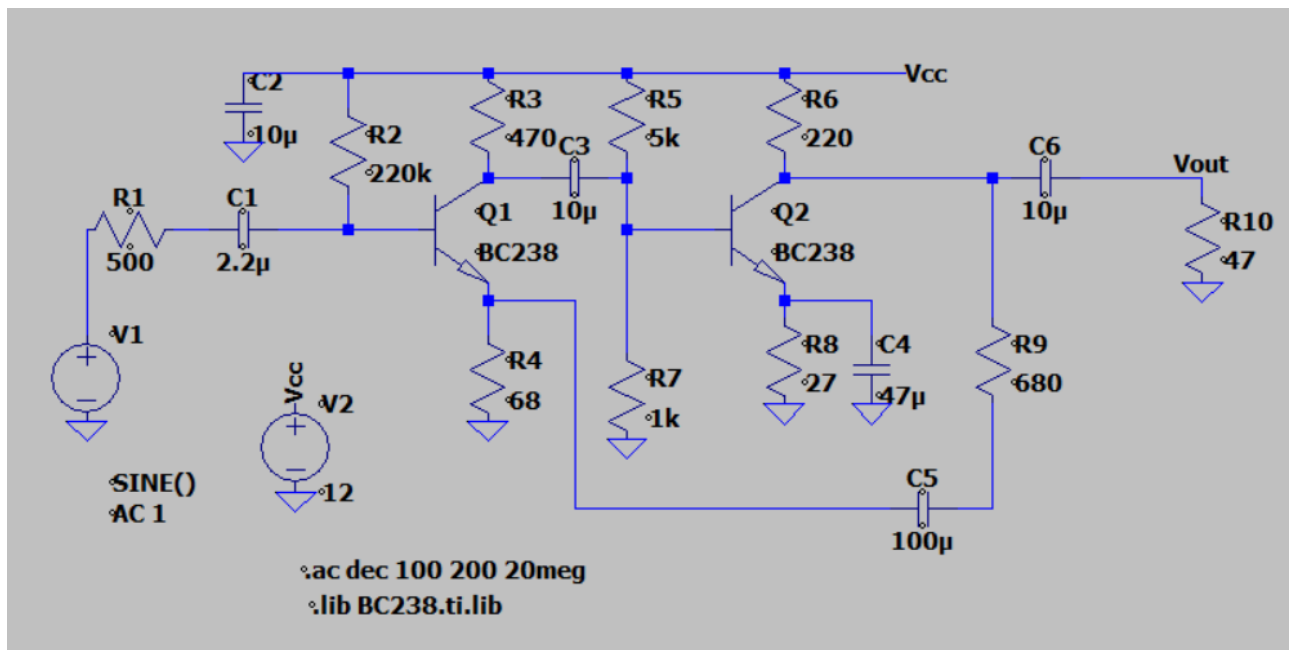

**Figure 2: The Final Circuit**

Here are the output voltage plots when the input voltage is  $0.2\text{ V}_{pp}$  and has a frequency of  $200\text{ kHz}$  (**Figures 3.1 & 3.2**). You can see that the output voltage is nearly  $2V_{pp}$  at these conditions.

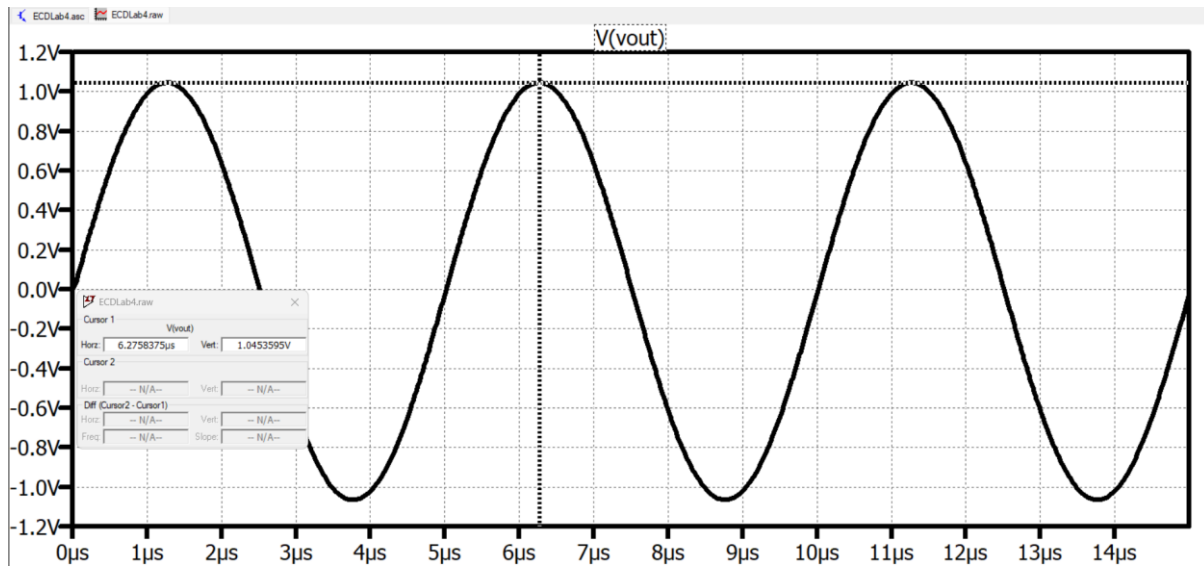


Figure 3.1: The Output Voltage being nearly 2Vpp when the input is 0.2Vpp 200kHz.

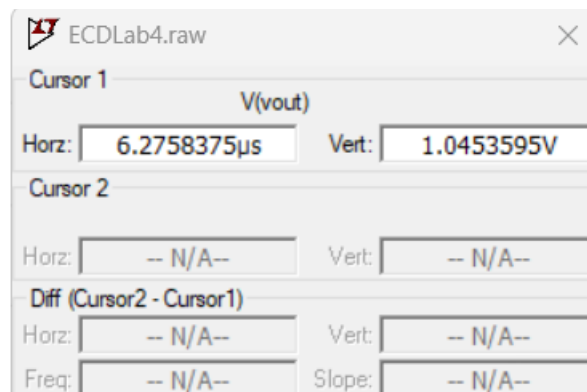


Figure 3.2: The Output voltage is 2.09 Vpp

Now I will show each of these 3 steps one by one (**Figure 4**).

Show that

1. The current consumption is less than 70mA
2. The small-signal bandwidth is at least 2KHz-2MHz while the mid-band gain is 20dB±0.5dB (by AC analysis)
3. The harmonic content of the output voltage is better than -30dBc with 0.1V peak input signal at 200KHz.

Figure 4: Three Requirements the Circuit Should Meet

### Condition 1:

Here you can see the current consumption of the circuit from the power source (**Figure 5**). As you can see, the current does not exceed 62.4mA which is well under the 70mA limit.

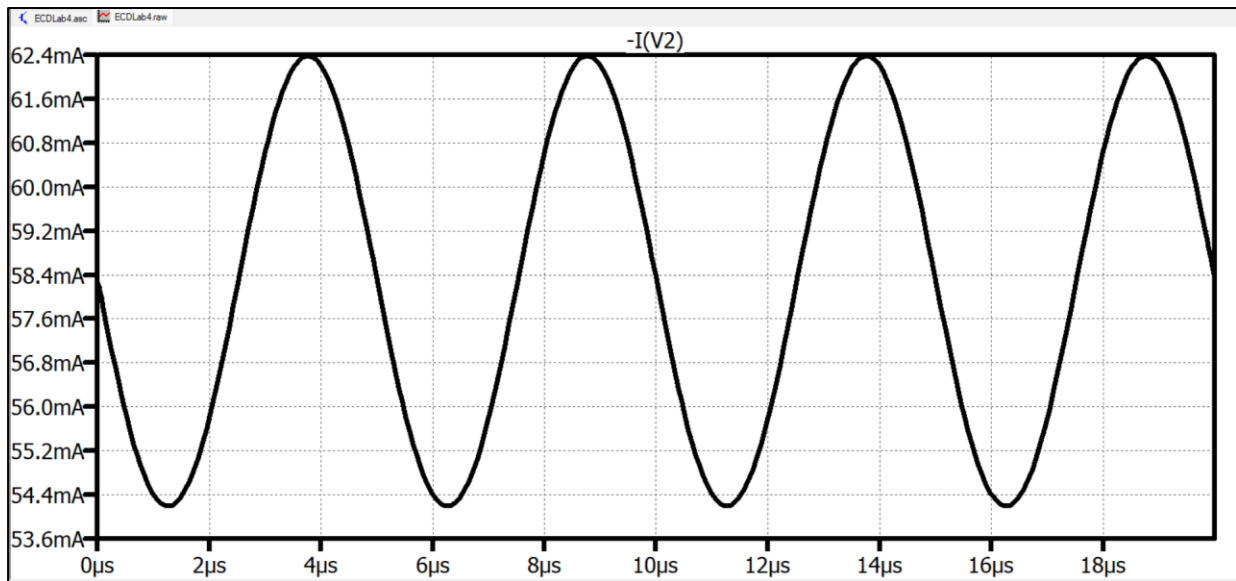


Figure 5: The Current Drawn from the 12V DC power source

### Condition 2:

To meet this condition, I applied an AC analysis to the circuit. Here is the new circuit and the results (**Figures 6.1 to 6.4**). As you can see the mid-band gain is at max 20.39dB which is within the limits. Also, the Mid-band gain does not drop below 19.5dB at 2kHz and 2MHz.

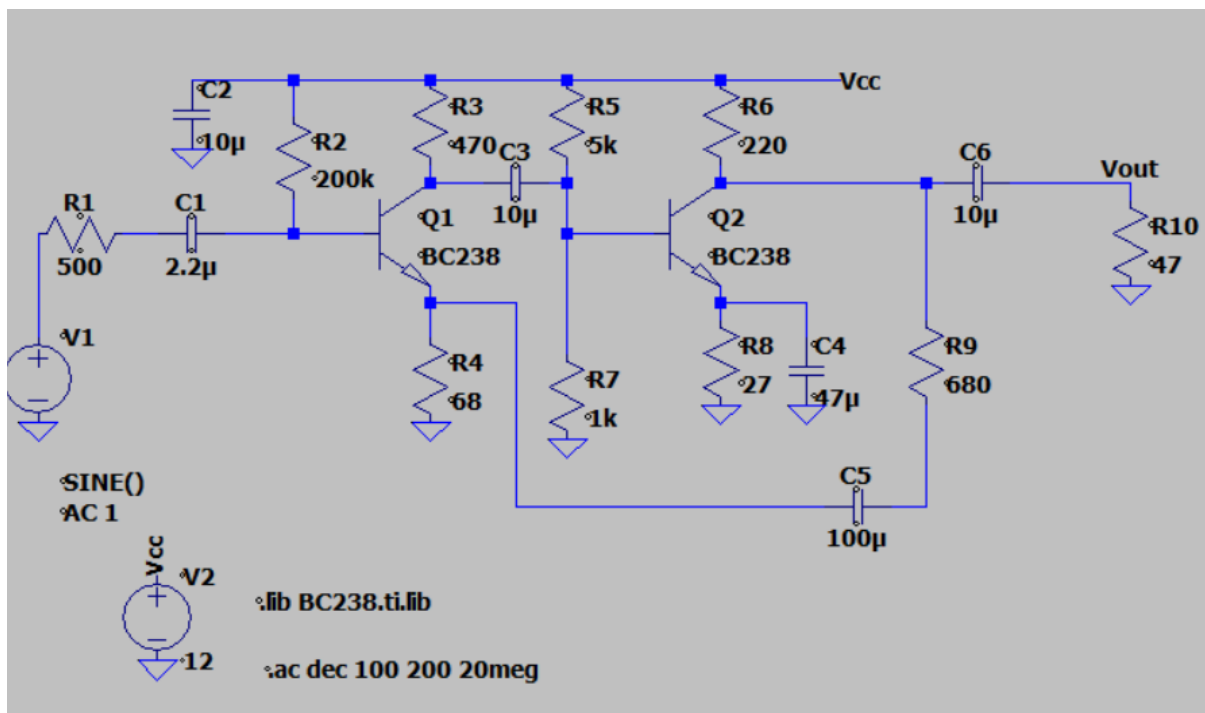


Figure 6.1: The AC Analysis Circuit

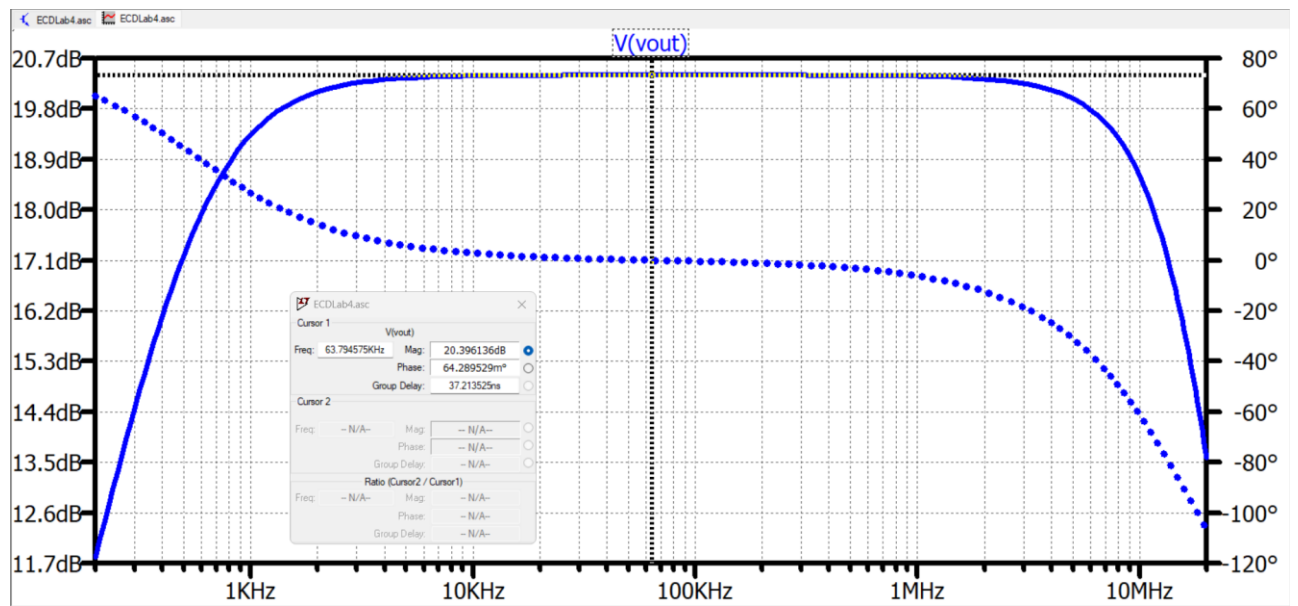


Figure 6.2: The Gain vs Frequency Plot

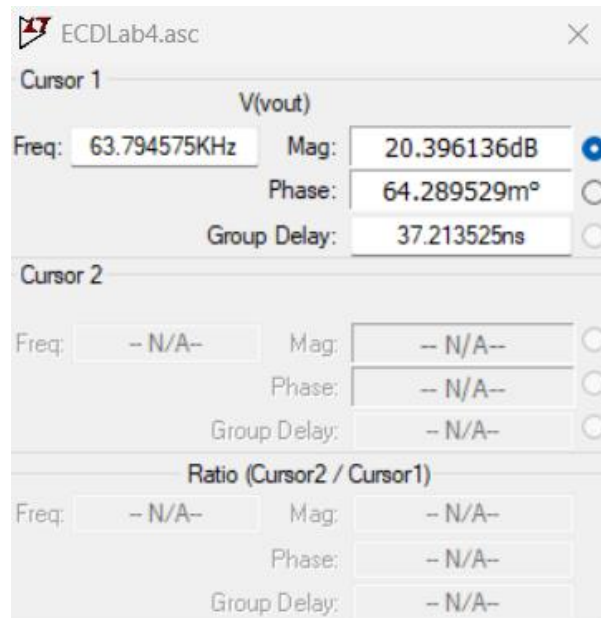


Figure 6.3: The Gain being maximum 20.39dB at the Wide-Band

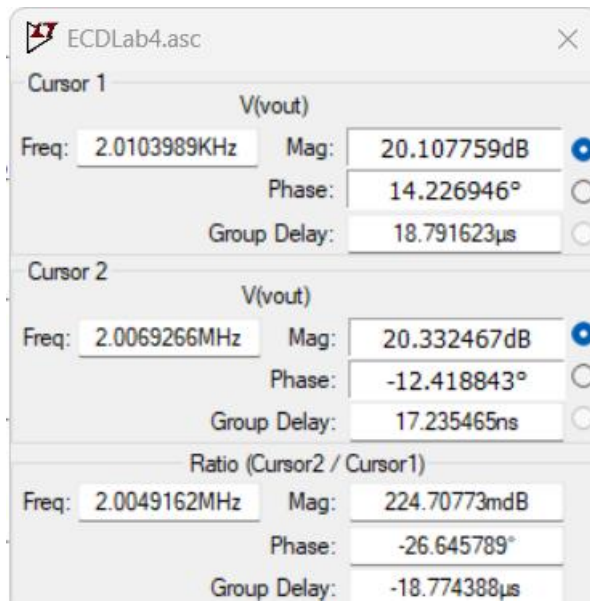


Figure 6.4: The Gain being 20.10dB at 2kHz and 20.33dB at 2MHz

### Condition 3:

FFT analysis was applied to Figure 3.1 with 100 periods and the following graph was obtained (**Figures 7.1 & 7.2**). As you can see, the difference between the main signal and the highest harmonic is 48dB, which is well above the minimum limit.


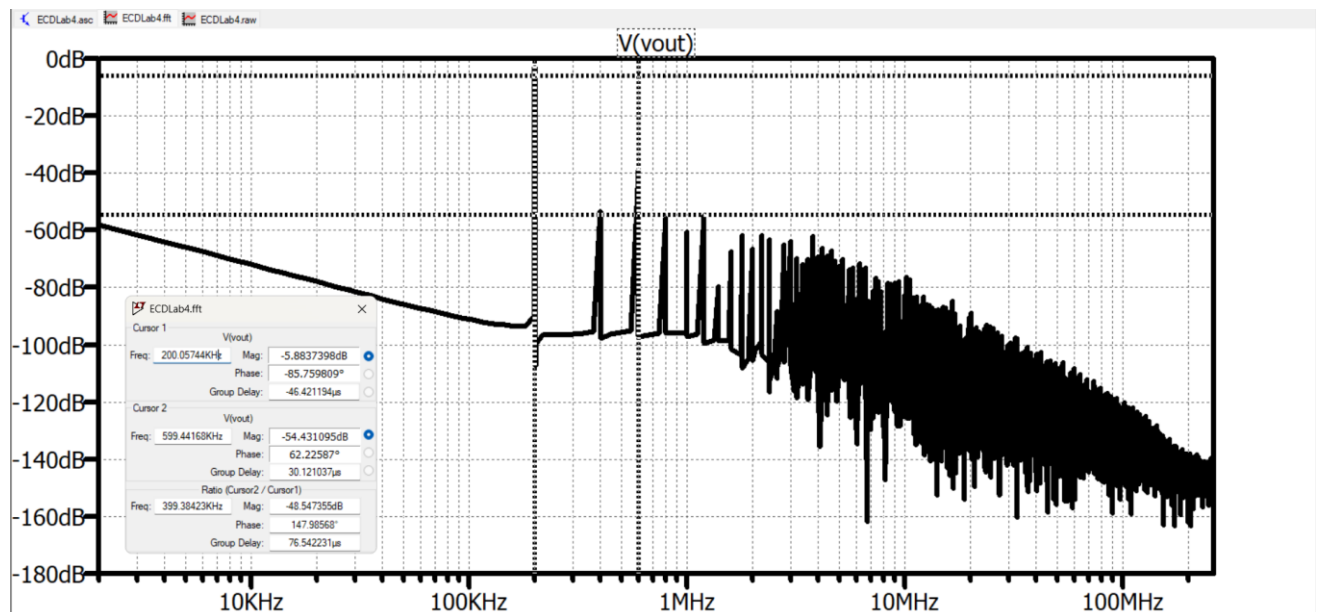


Figure 7.1: The FFT of the Output Voltage

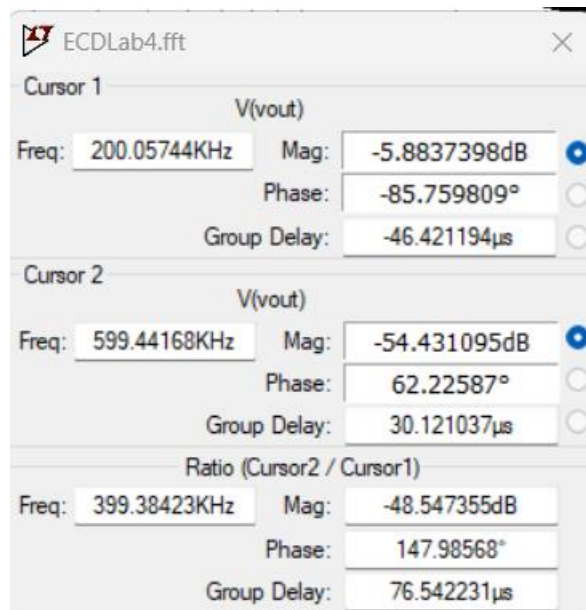

**Figure 7.2: The difference between the main signal and the highest harmonic being 48dB**

Now let's check one by one 3 other measurements that we should determine according to the lab manual (**Figure 8**):


**Determine**

4. The small-signal input impedance of the amplifier at 200KHz (the adjusted value of  $R_s$  in AC analysis until the voltage gain drops by 6dB compared to  $R_s=0$ )
5. The small-signal output impedance of the amplifier at 200KHz (the adjusted value of  $R_L$  in AC analysis until the voltage gain drops by 6dB compared to  $R_L=\infty$ )
6. The phase margin of the open-loop system.


**Figure 8: Conditions 4, 5 and 6**

**Condition 4:**

To measure the small-signal input impedance of the amplifier at 200kHz, I gradually incremented  $R_s$  until the gain at 200kHz was 14.45dB -6dB lower than the initial value of the gain when  $R_s$  is zero, 20.45dB. The gain was 14.25dB when the input resistance was 69kΩ. So, small-signal input impedance of the circuit is nearly 69kΩ. Here you can see the gain plots when  $R_s$  is 69kΩ and shorted: (**Figures 9.1 to 9.4**)

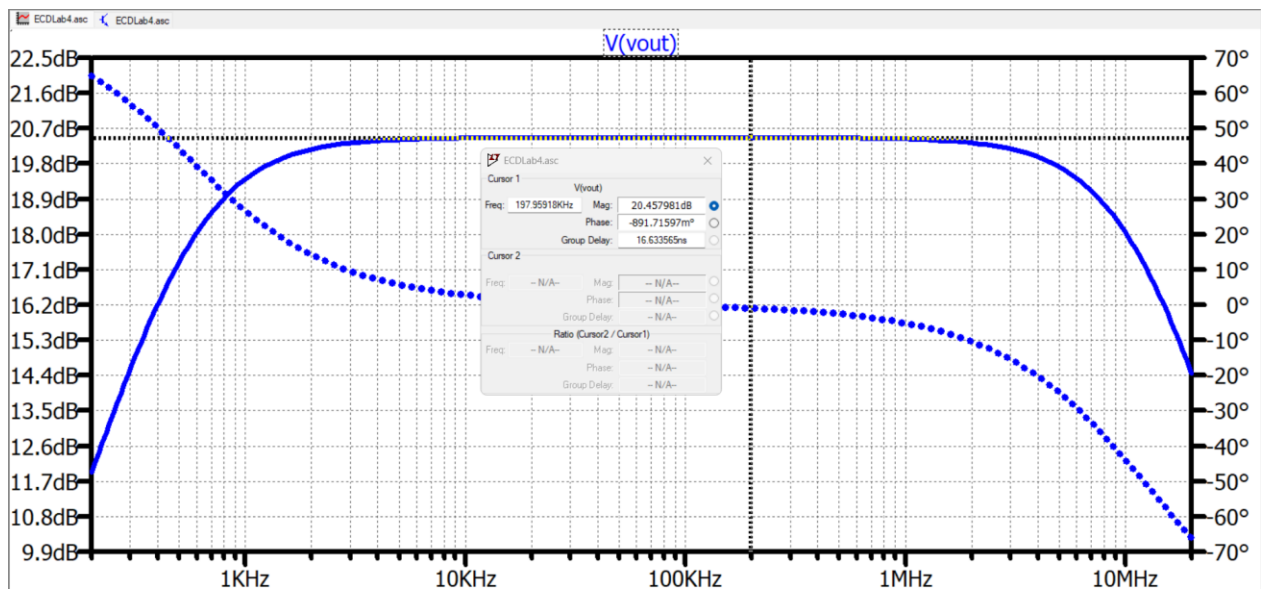


**Figure 9.1: The AC Analysis when  $R_s$  is Shorted**

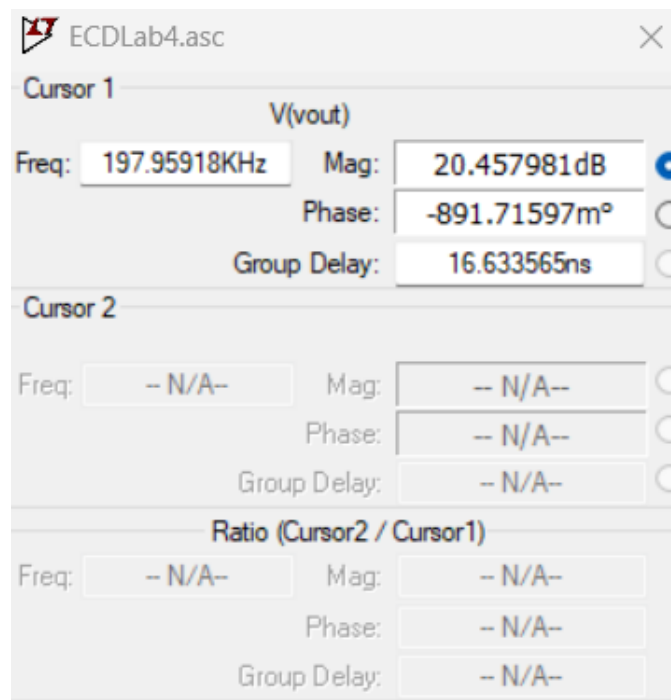


**Figure 9.2: The Gain is 20.45dB when  $R_s$  is Shorted**



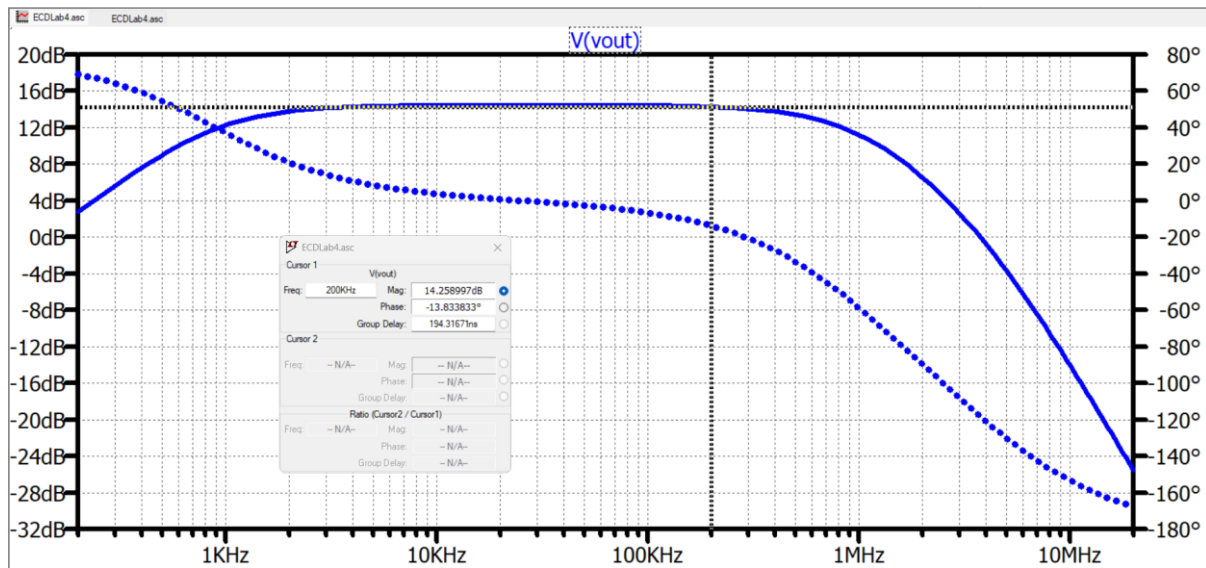

**Figure 9.3: The AC Analysis when  $R_s$  is  $69\text{k}\Omega$**

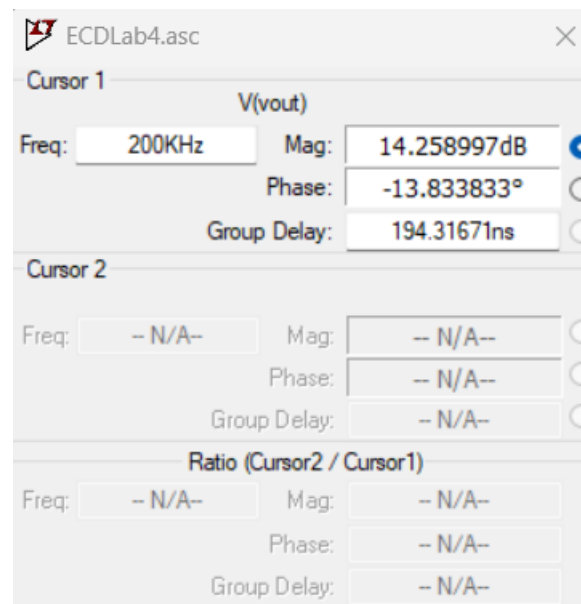


**Figure 9.4: The Gain is 14.25dB when  $R_s$  is  $69\text{k}\Omega$**


### Condition 5:

To measure the small-signal output impedance of the amplifier at 200kHz, I gradually decremented  $R_l$  until the gain at 200kHz was 15.68dB -6dB lower than the initial value of the gain when  $R_l$  is open-circuited, 21.68dB. The gain was 15.46dB when the output resistance

was  $7.2\Omega$ . So, small-signal input impedance of the circuit is nearly  $7.2\Omega$ . Here you can see the gain plots when  $R_I$  is  $7.2\Omega$  and open-circuited (**Figures 10.1 to 10.4**):

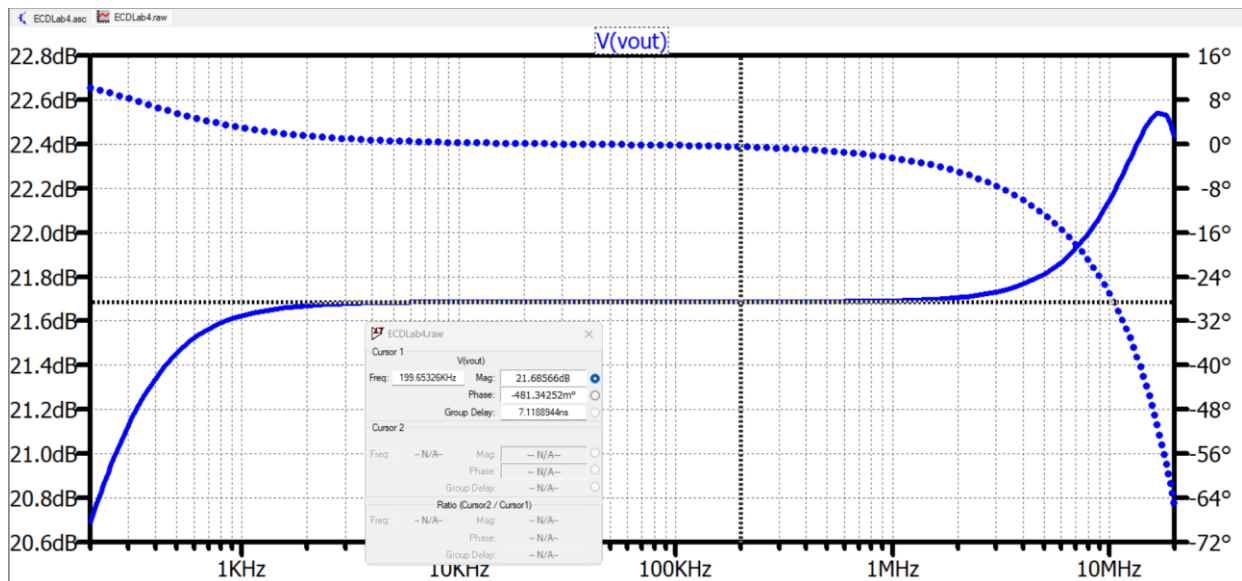

**Figure 10.1: The AC Analysis when  $R_I$  is Open Circuit**

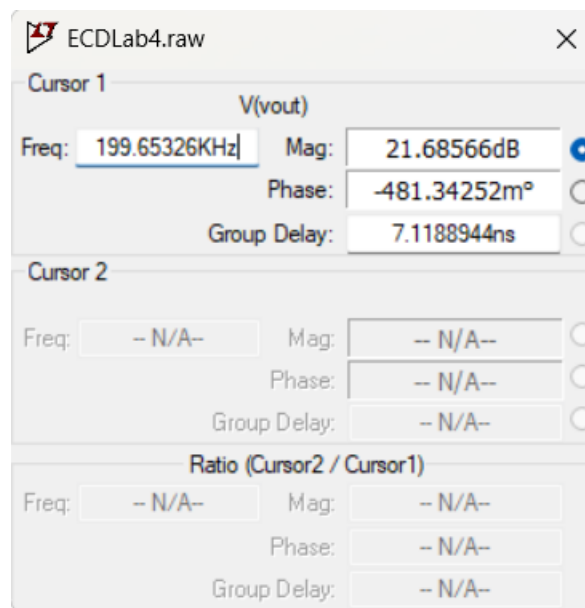

**Figure 10.2: Gain is 21.68dB when  $R_I$  is open-circuit**

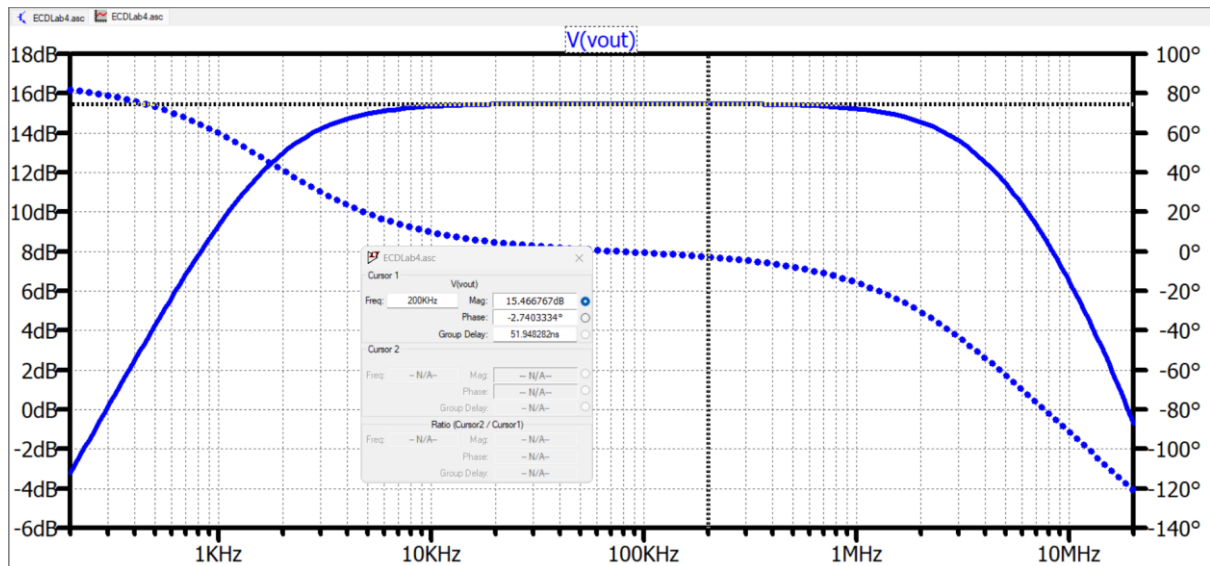


Figure 10.3: The AC Analysis when  $R_I$  is 7.2 Ohms

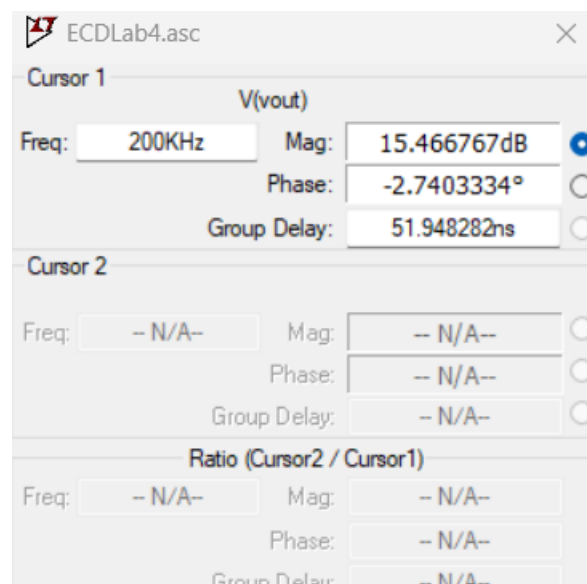


Figure 10.4: Gain is 15.46dB when  $R_I$  is 7.2 Ohms

### Condition 6:

To measure the phase margin of the open loop system, I changed and used this circuit (Figure 11). Here are my results (Figures 12.1 & 12.2). The phases are above the  $-360^\circ$  instability limit. No problem with phase shifts.

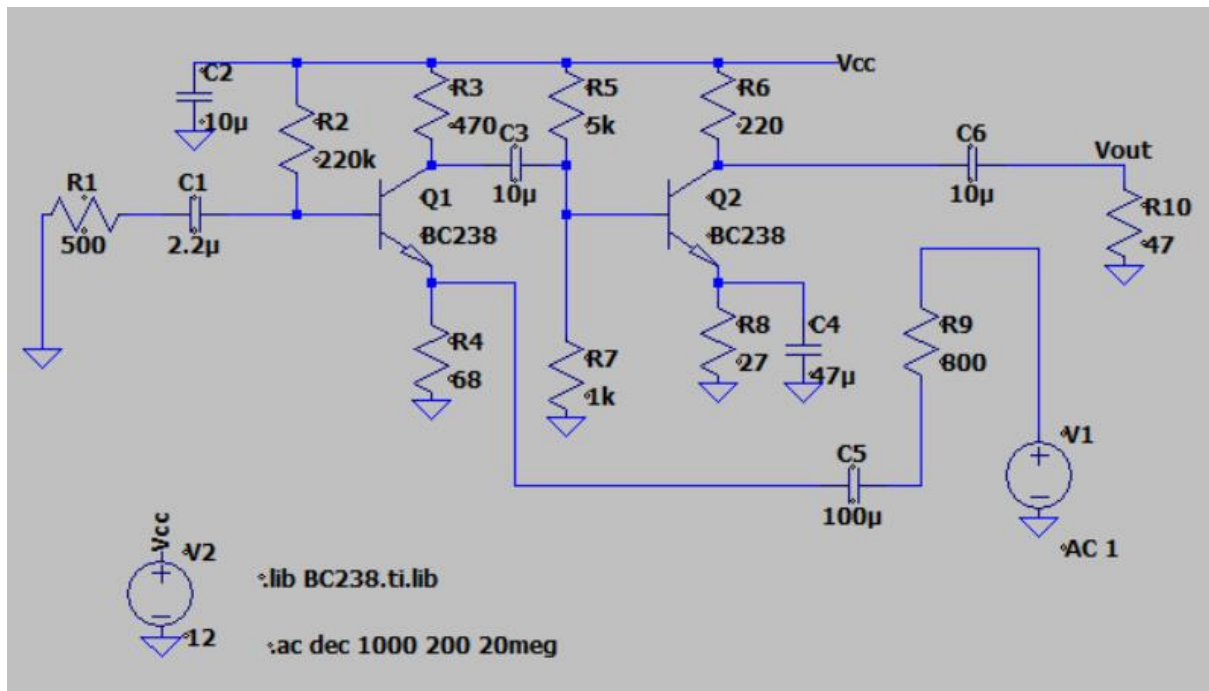


Figure 11: The New Circuit


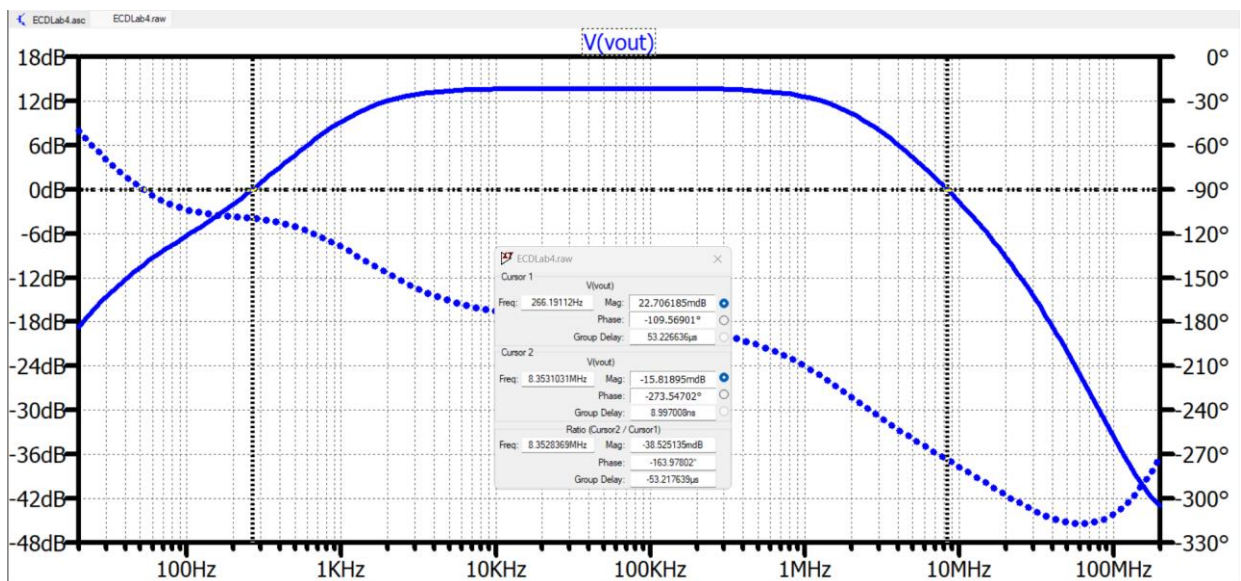


Figure 12.1: The Gain Plot

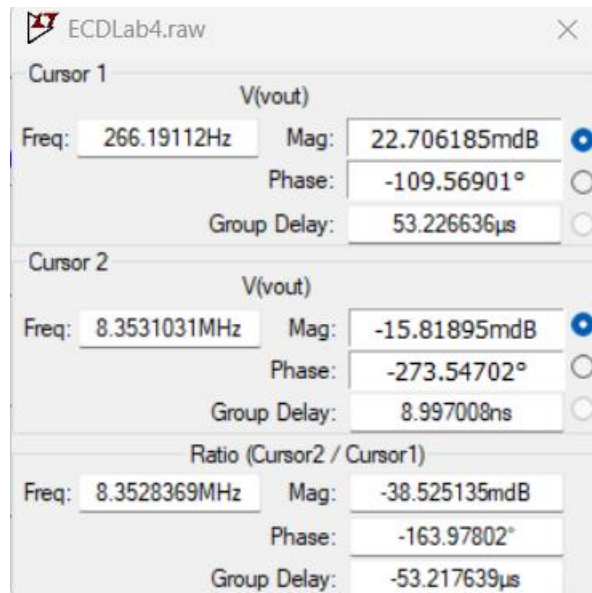

**Figure 12.2: The Phase at 266Hz (0dB) is  $-109^\circ$ ; The Phase at 8.35MHz (0dB) is  $-273^\circ$ .**

## Conclusion:

This lab's main aim was designing a two-stage amplifier with feedback to achieve a low output impedance and a flat gain.

The software part was successful. All the specifications and requirements were met.