

Bilkent University

Electrical and Electronics Department

EE313-02 Lab 1 Preliminary Report:

**“Diode Characterization and Differential
Temperature Sensor”**

28/09/2024

Fatih Mehmet Çetin - 22201689

Introduction:

This experiment consisted of two parts: A and B. In part A, we were asked to design a method to measure I_s of a p-n diode, 1N4148. In part B, we were asked to design a differential temperature sensor using the temperature dependence of a diode forward voltage under constant current with certain specifications.

In the lab manual, we were given the following recommended circuit for part B (**Figure 1.1**):

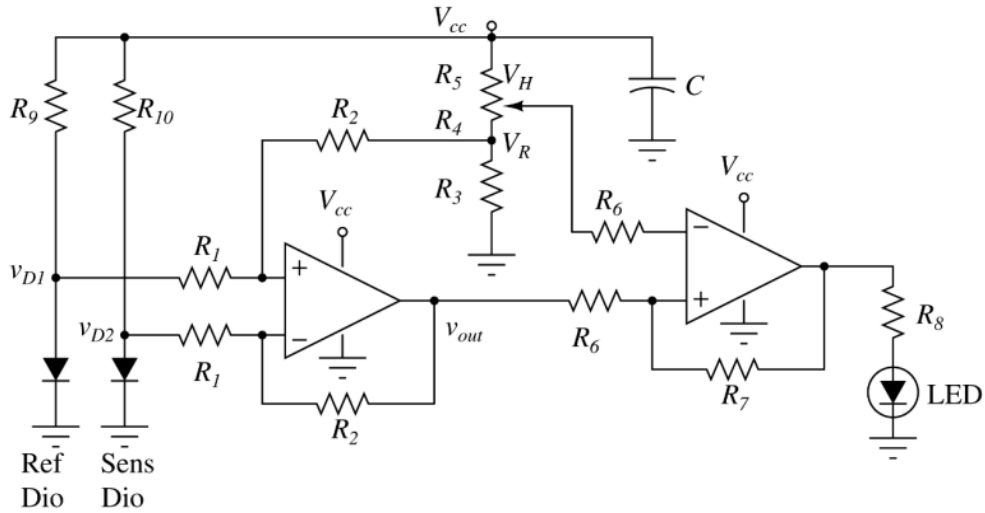


Figure 1.1: The Example Circuit in the Lab Manual for Part B

Simulation&Analysis:

Part A:

In this part of the experiment, we were asked to design a method to measure I_s of a p-n diode, 1N4148. The mathematical relationship between I_s and I_d is given in (1&2) where n is 1.752.

$$I_D = I_s \cdot \left(e^{\left(\frac{V_d}{n \cdot V_T} \right)} - 1 \right) \quad (1)$$

$$V_T = \frac{kT}{q} \quad (2)$$

The LTSpice circuit and simulation for Part A can be seen here (**Figures 2.1&2.2**):

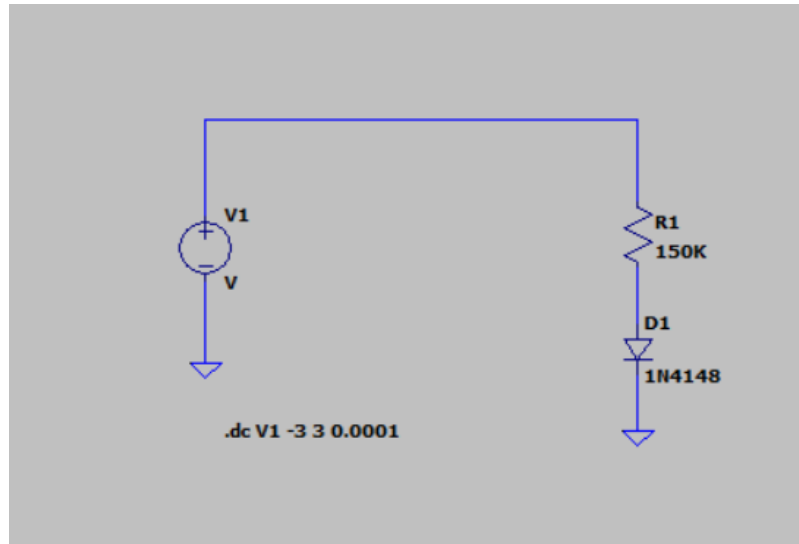


Figure 2.1: The LTSpice Circuit for I_s Analysis

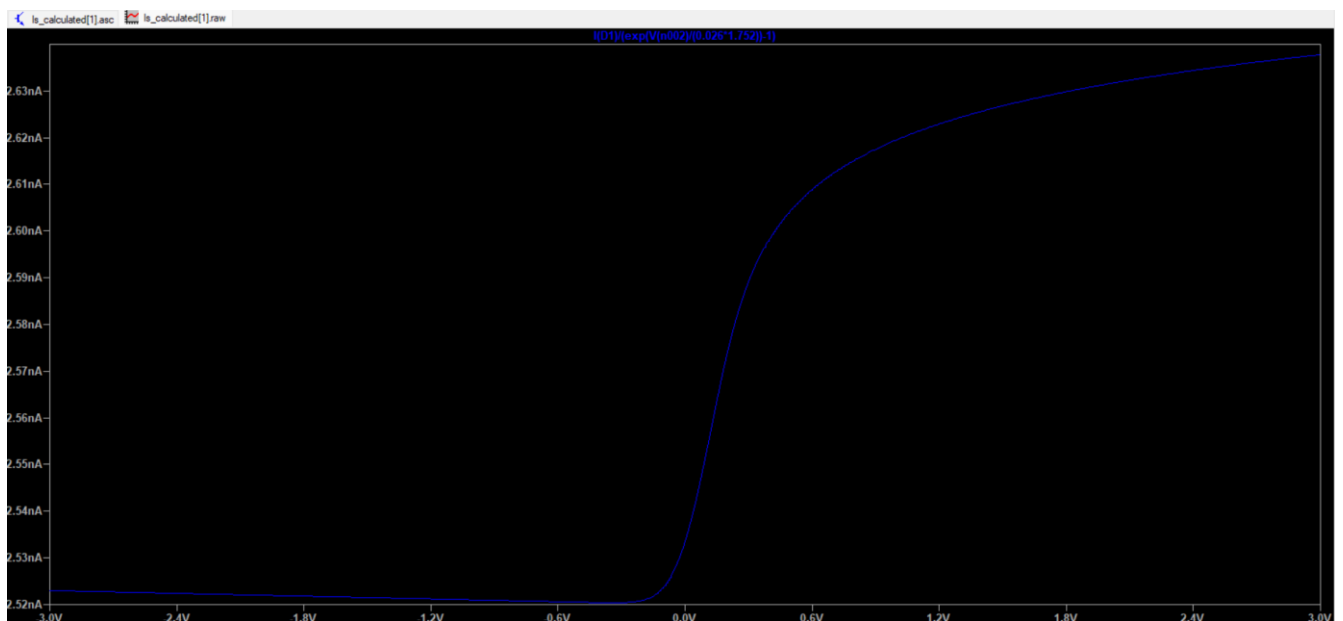


Figure 2.2: The LTSpice Simulation for I_s

It can be observed in the results that reverse bias region has 2.52nA I_s , as expected.

Part B:

In this part of the experiment, we were asked to design a differential temperature sensor using the temperature dependence of a diode forward voltage under constant current with certain specifications.

Since my Bilkent ID number ended with number 9, the DC supply voltage I used was 14V. Here is the overall circuit I used for the part B of the experiment (**Figure 2.3**):

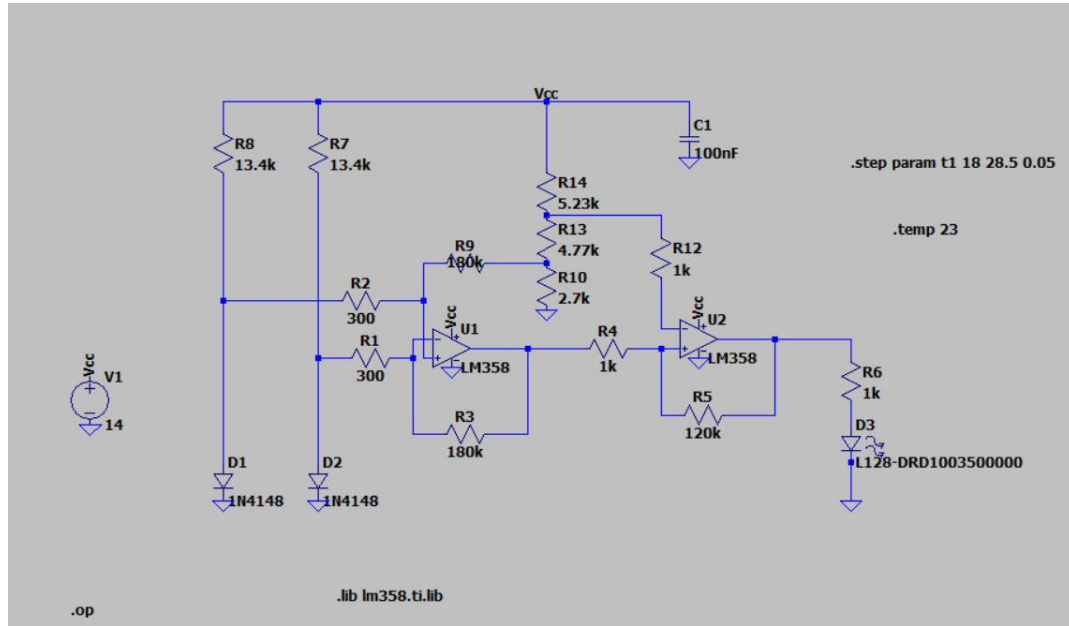


Figure 2.3: The overall circuit I used for the part B of the experiment

There are 4 requirements that the circuit should meet. These were given in the lab manual (**Figure 2.4**):

1. When both diodes are at room temperature ($V_{D1}=V_{D2}$), the output voltage, V_{out} , should be at $(V_{cc}-2)/4$
2. The output voltage should show the temperature difference between the room temperature and the temperature of the sensor diode in degrees with a 10% tolerance. For example, if the sensor diode is +1-degree warmer, V_{out} should change by +1V.
3. A red LED should turn on when the sensor's temperature exceeds $+5\pm0.5^{\circ}\text{C}$ the room temperature.
4. The LED should never flicker around the thresholds: It should have a 0.1°C (0.1V) hysteresis.

Figure 2.4: The Requirements the Circuit should Meet

Here you can see the simulation results for each criterion (**Figures 2.5 to 2.7**):

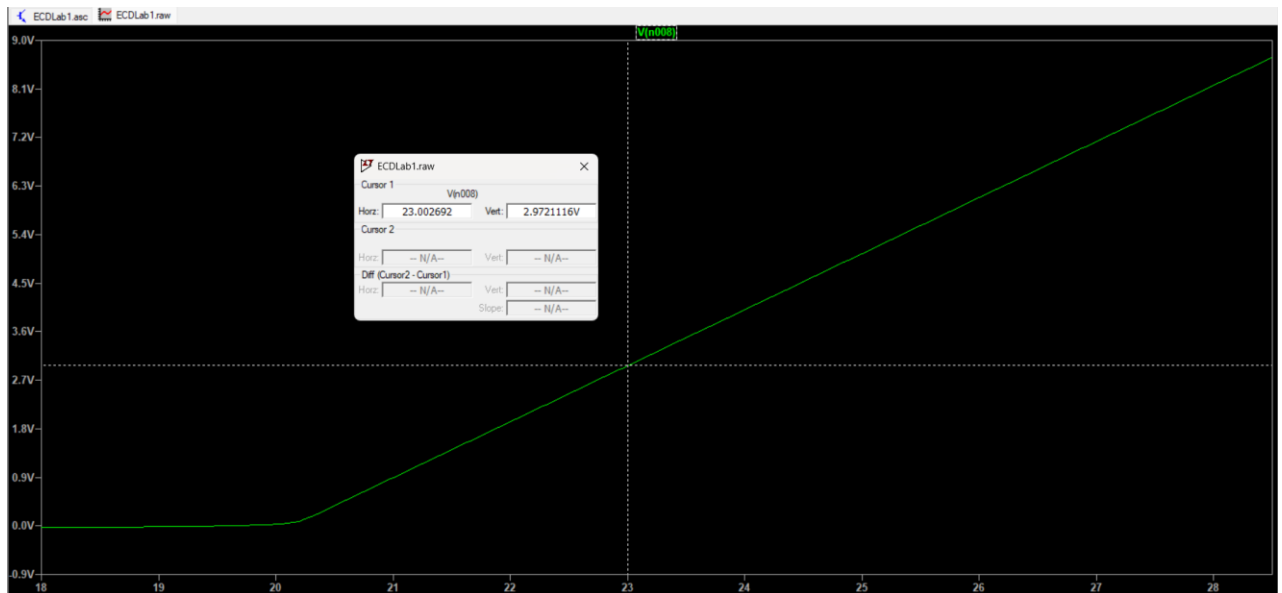


Figure 2.5 (Criterion 1): Output Voltage being 2.97 Volts as expected when both diodes are at 23°C

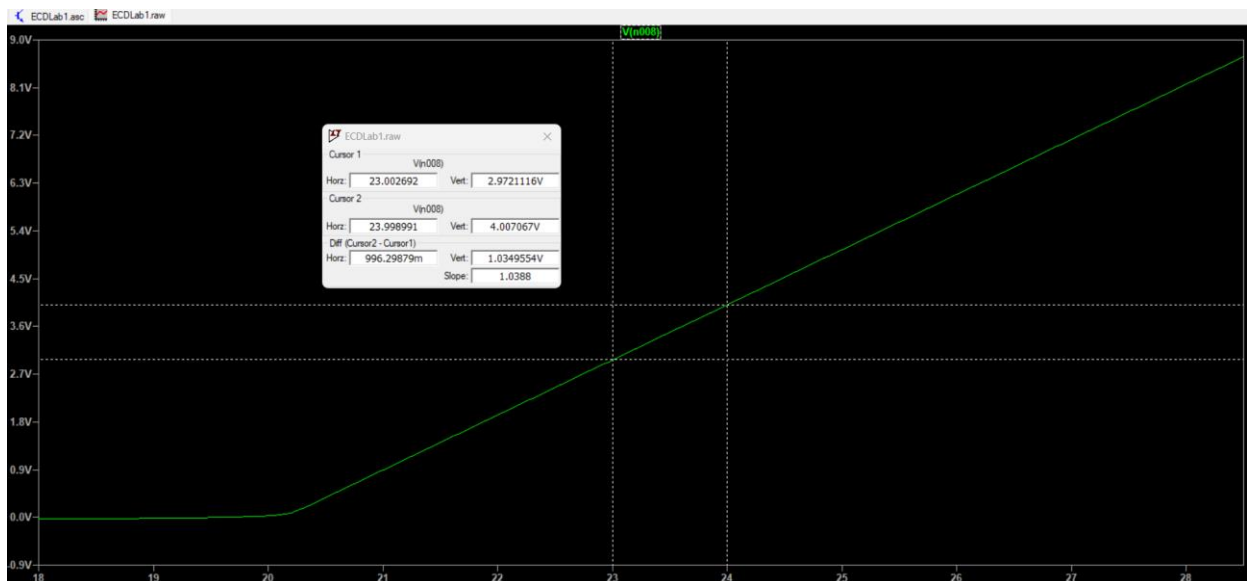


Figure 2.6 (Criterion 2): The Voltage Difference being 1 Volt when there is a 1°C Difference Between the Diodes as expected

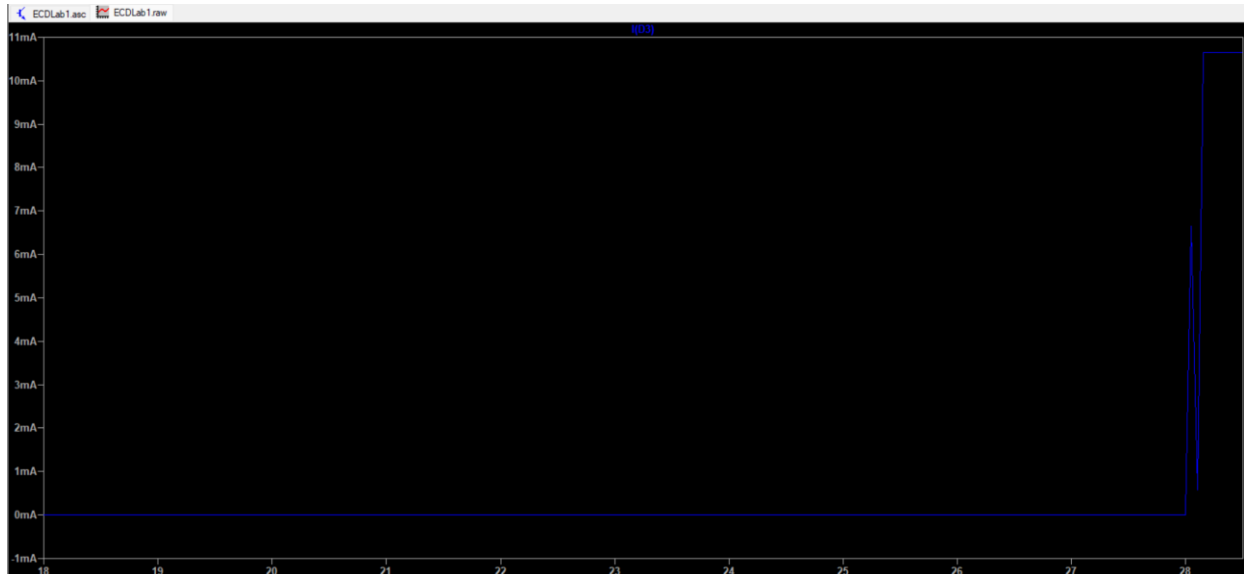


Figure 2.7 (Criterion 3): The current on the LED rising up when there is a 5°C difference between two diodes as expected – one is 23°C, the other is 28°C

For criterion 4, the equation for the hysteresis values given to us in the lab manual is given in (3):

$$(V_{cc} - 2) \cdot \left(\frac{R_7}{R_6}\right) = \text{Hysteresis Value} \quad (3)$$

The values I selected for R7 and R6 are 120kΩ and 1kΩ respectively. Therefore, the hysteresis value is 0.1 Volts as required.

Here you can see the output voltage when two diodes have the same temperature value (**Figure 2.8**):

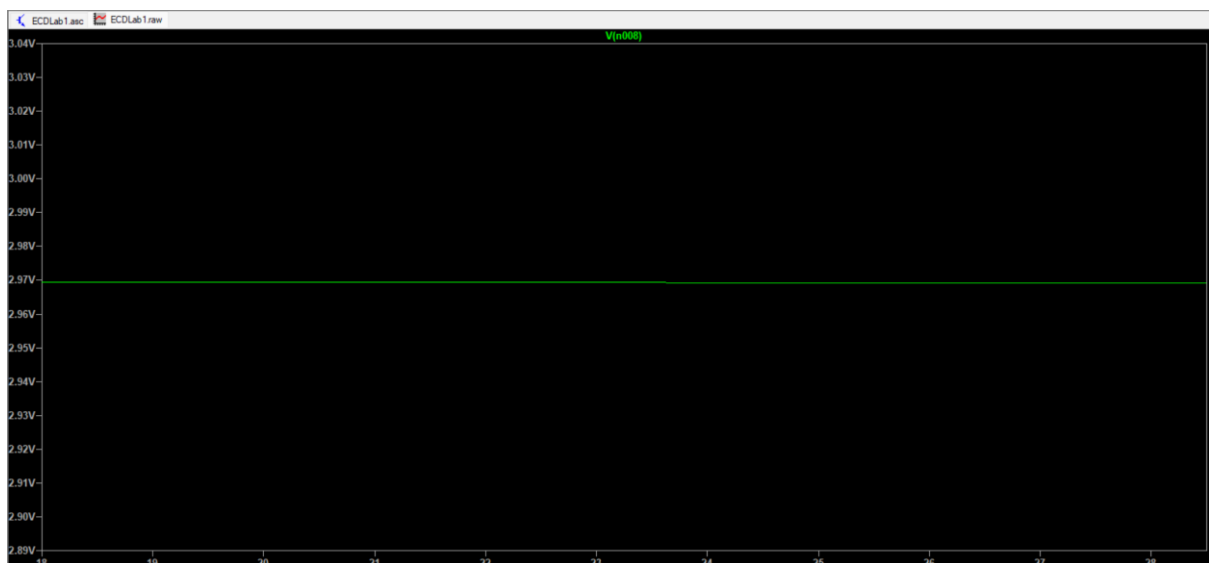


Figure 2.8: The Voltage Level is nearly 2.97 Volts for all temperatures between 18°C and 28°C.

2 1

B B

A A

C1 - 100nF capacitor
D1, D2 - 1N4148 diode
D3 - LED BRD1003500000

R1, R2 - 15.4k resistor
R3, R4 - 300 resistor
R5, R6 - 100k resistor
R7, R11, R13 - 1k resistor
R8 - 2.7k resistor
R9 - 4.77k resistor
R10 - 5.23k resistor
R12 - 120k resistor

U1 V+ : 14V	SIZE	FSCM NO.	DWG NO.	REV
U1 V- : 0V	SCALE		Sheet 1	

2 1

Conclusion & Thoughts on HW Part:

I believe the hardware implementation of this lab will be relatively easy but the precise measurements of the temperature of the diodes will be a hard challenge for both us and the TA's.

Appendices:

- 1- <https://diptrace.com/books/tutorial.pdf>